

Bridged Tee Dissipation

By Terry Cisco – Microwaves101.com

October 2015

$$P_{in} = 1 = (I_1)^2 * Z_{in} \quad \therefore I_1 = 1$$

$$P_{out} = (I_2)^2 * Z_{load} \quad \therefore P_{out} = (I_2)^2$$

$$(G)^2 \equiv P_{out}/P_{in} \quad \therefore G = I_2$$

$$(1) \quad -I_1 * 1 + (I_1 - I_3) * 1 + (I_1 - I_2) * R_2 = 0$$

$$(2) \quad (I_2 - I_3) * 1 + I_2 * 1 + (I_2 - I_1) * R_2 = 0$$

$$(3) \quad I_3 * R_1 + (I_3 - I_2) * 1 + (I_3 - I_1) * 1 = 0$$

$$\text{Eq (1) becomes} \quad I_3 = (1 - G) * R_2$$

$$\text{Eq (2) becomes} \quad I_3 = (2 + R_2) * G - R_2$$

Hence:

$$I_1 = 1$$

$$I_2 = G$$

$$I_3 = (1 - G) * R_2$$

Combining Eqs 1 & 2 yields

$$(4) \quad R_2 = G/(1 - G) \quad \text{where} \quad G = 10^{-\text{attenuation}/20} \quad \text{and} \quad \text{attenuation is in dB}$$

$$\text{For } R_1: \quad I_3 = \frac{V_{in} - V_{out}}{R_1} = \frac{I_1 * 1 - I_2 * 1}{R_1} \quad \therefore$$

$$(5) \quad I_3 = (1 - G)/R_1$$

$$\text{Combining Eqs 1 & 5 yields} \quad I_3 = (1 - G)/R_1 = (1 - G) * R_2 \quad \therefore$$

$$(6) \quad R_1 * R_2 = 1$$

For dissipation

$$(7) \quad P_D^{R1} = (1 - G)^2 * R_2$$


$$P_D^{R2} = (1 - G)^2 / R_1 \quad \therefore$$

$$(8) \quad P_D^{R1} = P_D^{R2} \quad \text{because } R_2 = 1/R_1$$

For Z1 and Z2 dissipation

$$P_D^{Z1} = (I_1 - I_3)^2 * 1 \quad \therefore P_D^{Z1} = (1 - G)^2$$
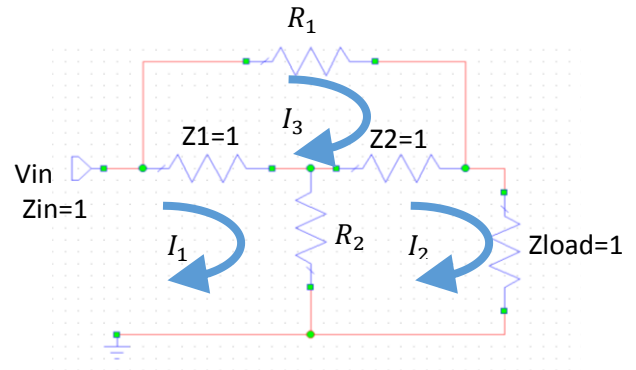
$$P_D^{Z2} = (I_2 - I_3)^2 * 1 \quad \therefore P_D^{Z2} = 0$$



Assumptions:

1. All resistances are normalized to Zo
2. Pin is 1 Watt
3. The circuit is designed to be matched.
4. Z1=Z2=Zo=1 by normalization